



American International University- Bangladesh
Department of Electrical and Electronic Engineering
 EEE2104: Electronic Devices Laboratory

Title: Study of Transistor Characteristics in Common Emitter Amplifier

Introduction:

A BJT is a three terminal semiconductor device. It is widely used in discrete circuits as well as in integrated circuits. The main applications of BJTs are analog circuits. For example, BJTs are used for amplifiers in particular for high speed amplifiers. BJTs can be used for digital circuits as well, but most of the digital circuits are nowadays realized by field effect transistors (FETs). There are three operating modes for BJTs, the active mode (amplifying mode), the cut-off mode and the saturation mode. To apply a BJT as an amplifier, the BJT has to operate in the active mode. To apply a BJT as a digital circuit element, the BJT has to operate in the cut-off mode and the saturation mode.

The main objectives of this experiment are to-


1. become familiar with bipolar junction transistors (BJTs)
2. study the biasing of a Common Emitter (CE) Amplifier, and
3. obtain the input and output characteristics of a common-emitter based BJT circuits.

Theory and Methodology:

Device structure of bipolar junction transistors


Each BJT consists of two anti serial connected diodes. The BJT can be either implemented as an npn or a pnp transistor. In both cases, the center region forms the base (B) of the transistor, while the external regions form the collector (C) and the emitter (E) of the transistor. External wire connections to the p and n regions (transistor terminals) are made through metal (e.g. Aluminum) contacts.

A cross section of the two types of BJTs consisting of an emitter-base junction and a collector-base junction is shown in the figure below. An npn or a pnp transistors are called bipolar transistors because both types of carriers (electrons and holes) contribute to the overall current. In the case of a field effect transistor, either the electrons or the holes determine the current flow. Therefore a field effect transistor is a unipolar device. The current and voltage amplification of a BJT is controlled by the geometry of the device (for example width of the base region) and the doping concentrations in the individual regions of the device. In order to achieve a high current amplification, the doping concentration in the emitter region is typically higher than that of the base region. The base is a lightly doped very thin region between the emitter and the collector and it controls the flow of charge carriers from the emitter to collector region.

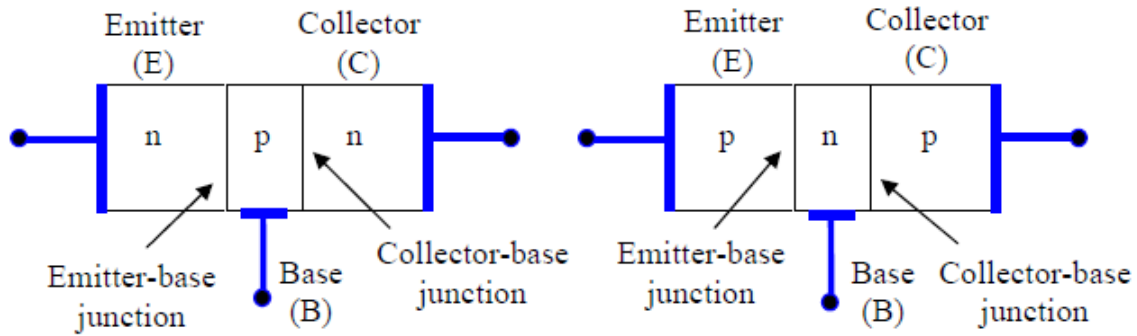


Circuit Configuration:

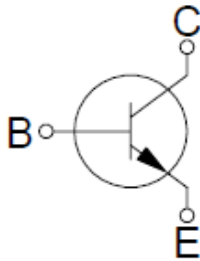
The following figures show the symbol for the npn transistor and pnp transistor. The emitter of the BJT is always marked by an arrow, which indicates whether the transistor is an npn or a pnp transistor.




npn BJT symbol

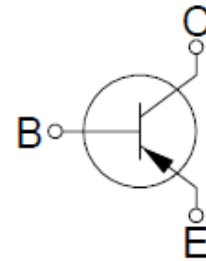


pnp BJT symbol

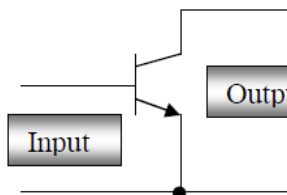

Common Emitter

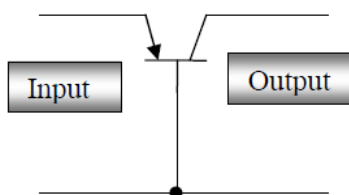

Common Base

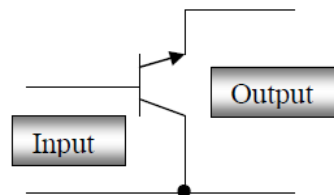

Common collector

There are three basic ways in which a BJT can be configured. In each case, one terminal is common to both the input and output circuit shown in figure above.

1. The common emitter configuration is used for voltage and current amplification and is the most common configuration for transistor amplifiers.
2. The common collector configuration often called an emitter follower, since its output is taken from the emitter resistor. It is useful as an impedance matching device since its input impedance is much higher than its output impedance.
3. The common base configuration is used for high frequency applications because the base separates the input and output, minimizing oscillations at high frequency. It has a high voltage gain, relatively low input impedance and high output impedance compared to the common collector.

Biassing of Bipolar Junction Transistors:

In most of the cases, the BJT is used as an amplifier or switch. In order to perform these functions, the transistor must be correctly biased. Depending on the bias condition (forward or reverse) of each of the BJT junctions, different modes of operation of the BJT are obtained. The three mode are defined as follows:

1. **Active:** Emitter junction is forward biased, collector junction is reverse biased. The BJT operates in the active mode and the BJT can be used as an amplifier.
2. **Saturation:** Both the emitter and collector junctions are forward biased. If the BJT is used as a switch, the saturation mode corresponds to the on state of the BJT.
3. **Cut-off:** Both the emitter and collector junction are reverse biased. If the BJT is used as a switch, the cut-off mode corresponds to the off state of the BJT.

Input and Output Characteristics:

The input characteristics curves are plotted between I_B and V_{BE} keeping the voltage, V_{CE} , constant. The input characteristics look like the characteristics of a forward-biased diode. The base-to-emitter voltage varies only slightly. The input dynamic resistance is calculated from the ratio of the small change of base-to-emitter voltage to the small change of base current.

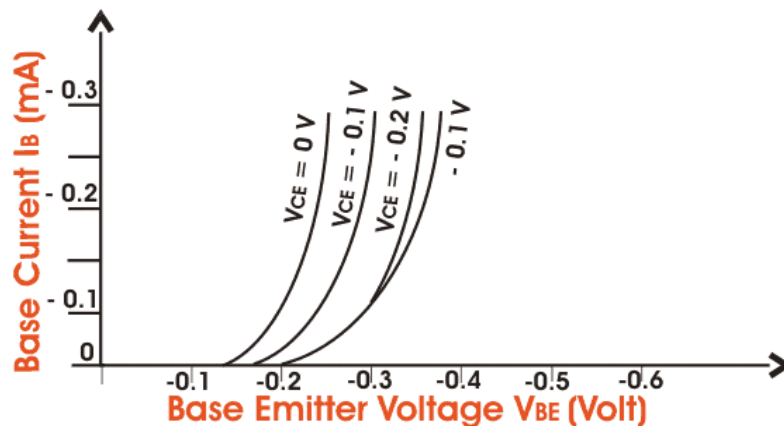


Fig: BJT Common Emitter Input Characteristics

The output characteristics curves are plotted between the collector current, I_C , and the collector-to-emitter voltage drop by keeping the base current, I_B , constant. These curves are almost horizontal. The output dynamic resistance again can be calculated from the ratio of the small change of emitter-to-collector voltage drop to the small change of the collector current.

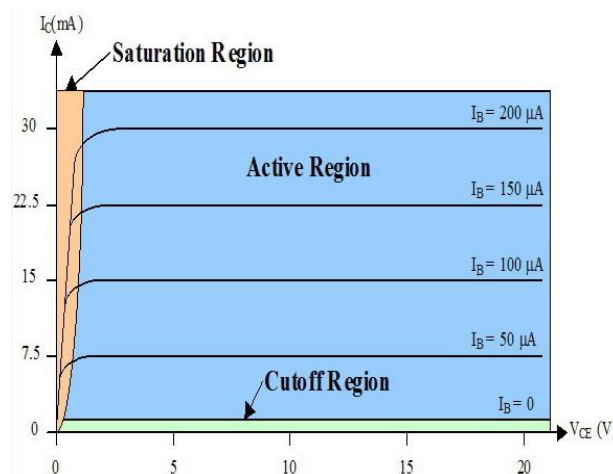


Fig: BJT Common Emitter Output Characteristics

Pre-Lab Homework:

You must solve the following questions and prepare a short report on it before the start of the lab.

Analyze the following common emitter circuit:

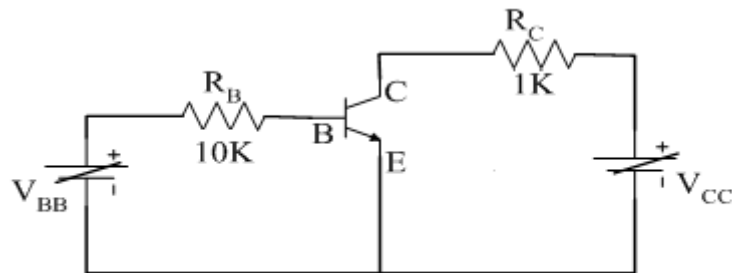


Figure: Transistor Characteristic in CE configuration.

1. Design the above common emitter circuit using PSpice simulation tool for 2N2222 transistor.
2. Determine the DC operation point values for V_B , V_C , V_{CE} , V_E , I_C , and I_B , where $V_{BB} = 0, 1, \text{ and } 2.5 \text{ V}$ and $V_{CC} = 8 \text{ V}$ and 16 V

Apparatus:

- | | | |
|-----------------------|---|----------------------|
| 1) Trainer Board | : | |
| 2) Transistor | : | C828 [1pc] |
| 3) Resistors | : | 1K Ω [1pc] |
| | | 10K Ω [1pc] |
| 4) DC Power Supply | : | |
| 5) Multimeter | : | |
| 6) Power Supply Cable | : | [2pc] |

Precautions:

Transistors are sensitive to be damaged by electrical overloads, heat, humidity, and radiation. Damage of this nature often occurs by applying the incorrect polarity voltage to the collector circuit or excessive voltage to the input circuit. One of the most frequent causes of damage to a transistor is the electrostatic discharge from the human body when the device is handled. The applied voltage, current should not exceed the maximum rating of the given transistor.

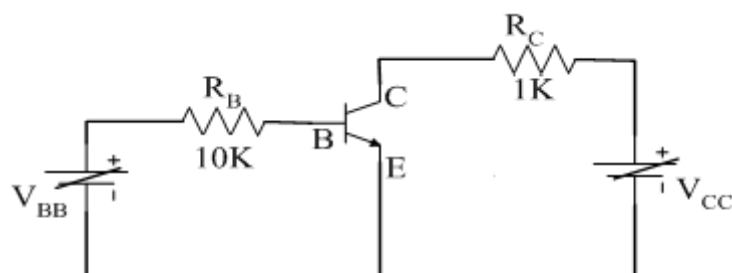
Experimental Procedure:**Circuit Diagram:**

Figure: Transistor Characteristic in CE configuration.

1. Identify the terminals of the transistor and record the value of Beta.
2. Make the circuit connections as shown in the above figure.
3. For input characteristics first fix the voltage V_{CE} and vary the voltage V_{BB} and calculate the Base current I_B using: $I_B = \frac{V_{BB} - V_{BE}}{10k}$
4. For output characteristics, first open the input circuit (i. e. to make $I_B = 0$). Vary the collector voltage V_{CC} in steps of 4V and calculate the Collector current I_C using: $I_C = \frac{V_{CC} - V_{CE}}{1k}$
5. Now close the input circuit and fix the base current I_B at $50\mu A$ by varying V_{BB} . Vary the voltage V_{CC} according to the table and calculate I_C in each step. Repeat the process for other values of I_B .
6. Plot the input and output characteristic graphs and locate the Q-point

Data Table:**1. Input Characteristics**

| $V_{CC} = 8V$ | | | $V_{CC} = 16V$ | | |
|---------------|----------|-------|----------------|----------|-------|
| V_{BB} | V_{BE} | I_B | V_{BB} | V_{BE} | I_B |
| 0v | | | 0v | | |
| 0.5v | | | 0.5v | | |
| 1v | | | 1v | | |
| 1.5v | | | 1.5v | | |
| 2v | | | 2v | | |
| 2.5v | | | 2.5v | | |

2. Output Characteristics

| $I_B = 0\mu A$ | | | $I_B = 50\mu A$ | | | $I_B = 100\mu A$ | | |
|----------------|----------|-------|-----------------|----------|-------|------------------|----------|-------|
| V_{CC} | V_{CE} | I_C | V_{CC} | V_{CE} | I_C | V_{CC} | V_{CE} | I_C |
| 0v | | | 0v | | | 0v | | |
| 4v | | | 4v | | | 4v | | |
| 8v | | | 8v | | | 8v | | |
| 12v | | | 12v | | | 12v | | |
| 16v | | | 16v | | | 16v | | |

Simulation and Measurement:

Compare the simulation results with your experimental data/ wave shapes and comment on the differences (if any).

Questions for report writing:

- 1) Plot the input $\{I_B \text{ vs } V_{BE}\}$ and output $\{I_C \text{ vs } V_{CE}\}$ characteristics as well as $\{I_B \text{ vs } I_C\}$ curves using Excel.
- 2) Simulate the circuit and submit simulated tables and graphs to be compared with the experimental graphs.

- 3) Show all calculations for theoretical values and submit tables and graphs to be compared with the experimental graphs.
- 4) Explain the behavior of the input and output characteristics in terms of the three regions of operation: cutoff, active, saturation.
- 5) What is the Q-point? Discuss its significance

Discussion and Conclusion:

Interpret the data/findings and determine the extent to which the experiment was successful in complying with the goal that was initially set. Discuss any mistake you might have made while conducting the investigation and describe ways the study could have been improved.

Reference(s):

1. Adel S. Sedra, Kenneth C. Smith, Microelectronic Circuits, Saunders College Publishing, 3rd ed., ISBN: 0-03-051648-X, 1991.
2. American International University–Bangladesh (AIUB) Electronic Devices Lab Manual.
3. David J. Comer, Donald T. Comer, Fundamentals of Electronic Circuit Design, John Wiley & Sons Canada, Ltd.; ISBN: 0471410160, 2002.